

Laboratory Session: Week 3: Transducers

Calpe_Khyle

Kuo_Calvin

Electro-Optic Transducers

Photoconductors

Photoconductor Resistance

In darkness: $\sim 1.2 \text{ M}\Omega$


In bright light: $1.63 \text{ k}\Omega$

Light-Emitting Diodes (LEDs)

WORK SHEET HERE:

<u>Supply Voltage</u>	<u>Voltage_{Resistor}</u>	<u>Voltage_{LED}</u>	<u>Current_{LED}</u> (<u>$V_{\text{resistor}} / 1000$</u>)
0 V	0 V	0.006 V	0 A
0.5 V	0 V	.562 V	0 A
1.0 V	0 V	1.018 V	0 A
1.5 V	0 V	1.578 V	0 A
2.0 V	.006 V	2.072 V	$6 \cdot 10^{-6} \text{ A}$
2.5 V	.242 V	2.286 V	$2.42 \cdot 10^{-4} \text{ A}$
5.0 V	2.227 V	2.796 V	$2.23 \cdot 10^{-3} \text{ A}$
10 V	6.590 V	3.436 V	$6.59 \cdot 10^{-3} \text{ A}$
15 V	11.2 V	3.844 V	$1.12 \cdot 10^{-2} \text{ A}$

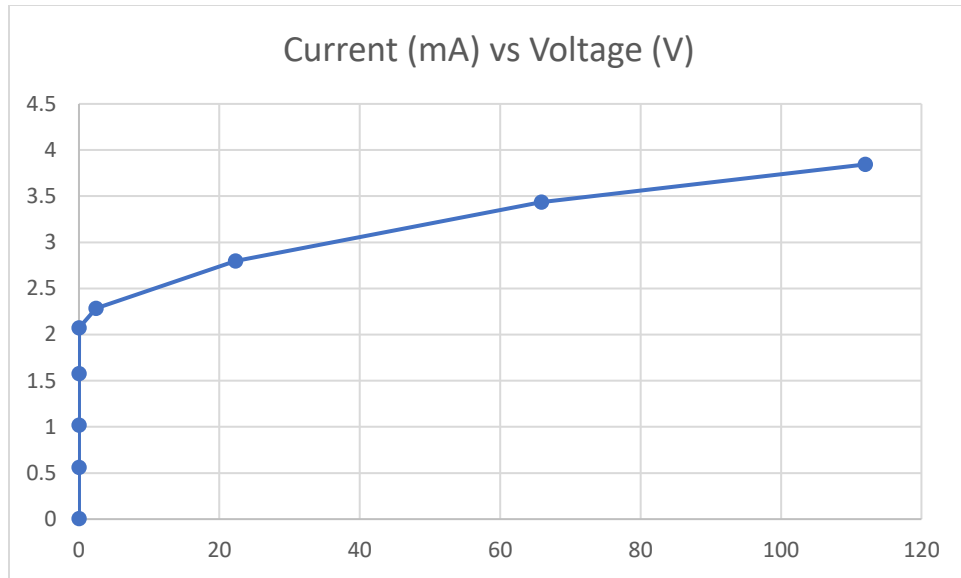At approximately what LED voltage does the LED start to glow? 2.0 V



Phototransistors

WORK SHEET HERE: (Use DMM for your voltage measurements only!)

	<u>100 KΩ</u>		<u>10 KΩ</u>	
	<u>Voltage</u>	<u>Calculated Current</u>	<u>Voltage</u>	<u>Calculated Current</u>
Object Above	1.543 V	1.543×10^{-5} A	0.107 V	1.07×10^{-5} A
No Object	0.005 V	5×10^{-8} A	0.143 V	1.43×10^{-5} A


Electro-Mechanical Transducers

Motors and Generators

WORK SHEET HERE:

<u>Duty Cycle %</u>	<u>Average Motor Volts</u>	<u>Motor Current Amps</u>
20	<u>1.314 V</u>	<u>0 A</u>
30	<u>1.859 V</u>	<u>0.08 A</u>
40	<u>2.185 V</u>	<u>0.08 A</u>
50	<u>2.729 V</u>	<u>0.08 A</u>
60	<u>3.275 V</u>	<u>0.08 A</u>
70	<u>3.821 V</u>	<u>0.08 A</u>

80	<u>4.369 V</u>	<u>0.08 A</u>
90	<u>4.916 V</u>	<u>0.08 A</u>
80	<u>4.579 V</u>	<u>0.08 A</u>
70	<u>3.824 V</u>	<u>0.08 A</u>
60	<u>3.275 V</u>	<u>0.08 A</u>
50	<u>2.736 V</u>	<u>0.08 A</u>
40	<u>2.185 V</u>	<u>0.08 A</u>
30	<u>1.636 V</u>	<u>0.08 A</u>
20	<u>1.089 V</u>	<u>0.08 A</u>
10	<u>771 mV</u>	<u>0 A</u>

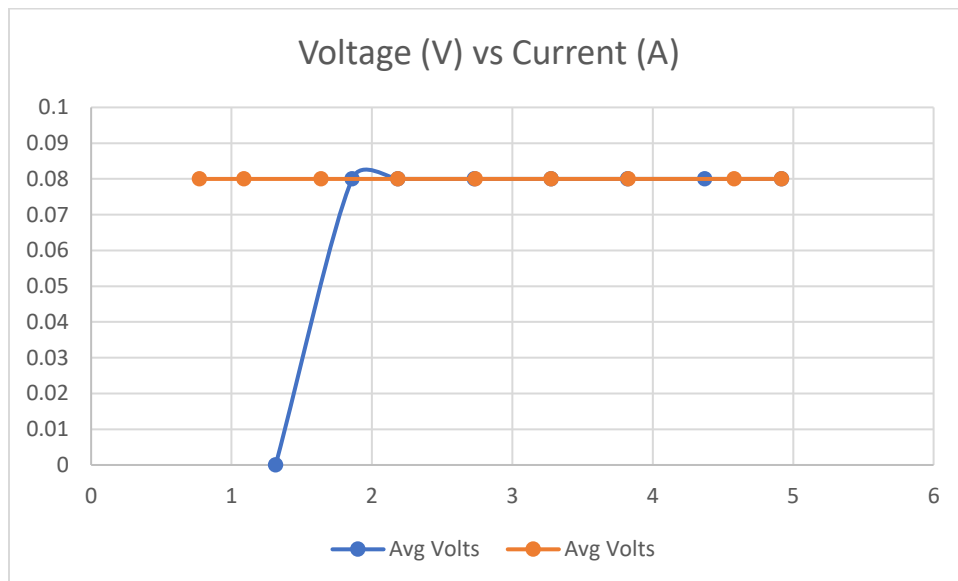

What voltage and current are required to just start the motor spinning? 0.1 V and 0.08 A