


Week 1 Prelab

Briefly answer the following questions.

Name: *Kyle Calpe*


UID: *405-016-683*

1. Identify the resistors:

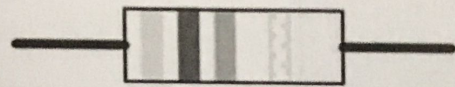

*Yellow-Violet-Orange-Gold*

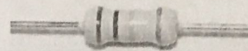
*47k*  $\Omega$  with a tolerance of  $\pm$  *5* %.



*Brown-Black-Yellow-Silver*

*100k*  $\Omega$  with a tolerance of  $\pm$  *10* %.

2.

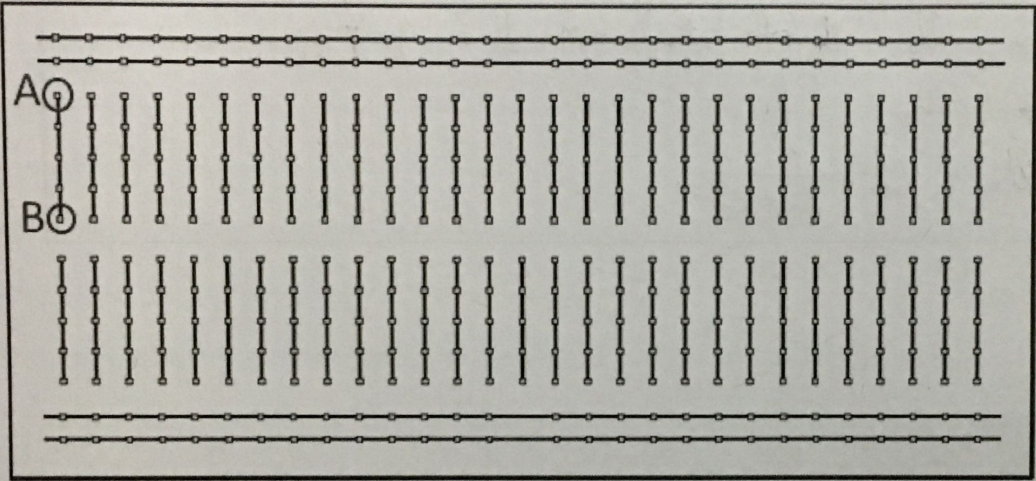


If a resistor is inserted into the breadboard with one leg at point A and one leg at point B, what resistance will an ohmmeter measure for that resistor? Why? What should you do instead to measure the proper resistance?


*The ohmmeter will measure 0  $\Omega$  because the current will travel through the strip as a result of current following the path of least resistance. Instead, the resistor must be connected between two different strips and then measured.*

3. Draw the I-V curves for the following diagrams


(a) Ideal voltage source

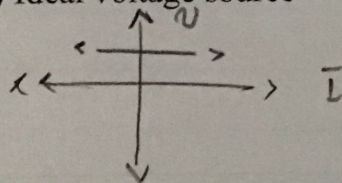


(b) Non-ideal voltage source

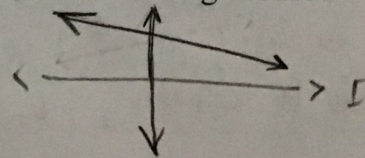

(c) Ideal current source

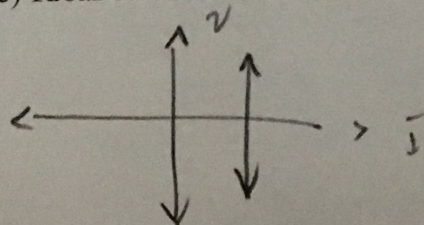


(d) Non-ideal current source

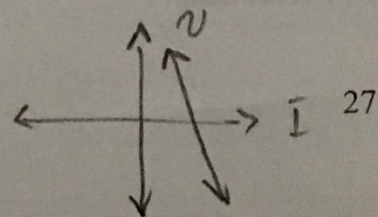



4. Prove the voltage and current divider equations: They are basic and very commonly used equations that you should memorize for use in all your future electronics courses.

### Voltage Divider

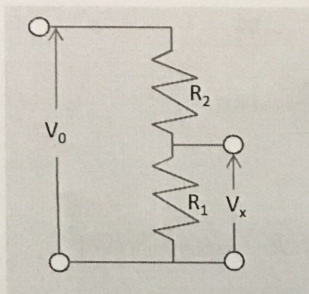


Problem: show that

$$V_x = V_0 R_1 / (R_1 + R_2)$$

#### YOUR SOLUTION HERE:

- ① The resistors are connected in series:  $R = R_1 + R_2$
- ② by Ohm's law:  $V_0 = I(R_1 + R_2) \Rightarrow I = \frac{V_0}{R_1 + R_2}$
- ③ By Ohm's law:  $V_x = I R_1$
- ④ Substitute:  $V_x = V_0 \frac{R_1}{R_1 + R_2}$

### Current Divider

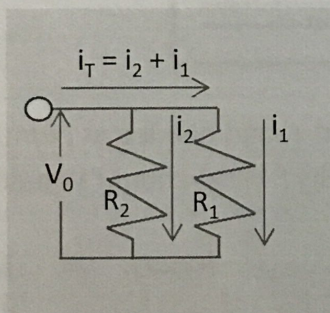

Problem: show that

$$I_1 = i_T R_2 / (R_1 + R_2)$$

#### YOUR SOLUTION HERE:

- ①  $R = \frac{R_1 R_2}{R_1 + R_2}$
- ②  $V_0 : i_2 R_2 = i_1 R_1$
- ③  $V_0 : i_T R = i_T \left( \frac{R_1 R_2}{R_1 + R_2} \right)$
- ④ By substitution,  $i_1 = i_T \left( \frac{R_2}{R_1 + R_2} \right)$

Week 1 Prelab End